



BOARD QUESTION PAPER: MARCH 2025

Electronics Paper - I

Time: 3 Hours**Max. Marks: 50****Instructions:**

- i. All questions are compulsory.
- ii. Figures to the right indicate full marks.
- iii. Draw neat labelled diagrams whenever necessary.
- iv. Use of logtable is allowed.

1. (A) Select correct alternatives from the following sub-question and rewrite the complete sentences.
 - (a) In a full wave bridge rectifier the ripple frequency is _____. (1)
 - (i) f
 - (ii) $2f$
 - (iii) $3f$
 - (iv) $4f$
 - (b) Loud Speaker is a _____ type of transducer. (1)
 - (i) Pressure
 - (ii) Temperature
 - (iii) Electro acoustics
 - (iv) None of these
 - (c) In fax machines for scanning _____ are used. (1)
 - (i) LEDs
 - (ii) LCDs
 - (iii) CCDs
 - (iv) None of these
 - (d) _____ multivibrator is an oscillator. (1)
 - (i) Astable
 - (ii) Bistable
 - (iii) Monostable
 - (iv) None of these
- (B) Attempt **any two** of the following:
 - (a) Explain the working of centre-tap full wave rectifier with neat diagram and wave-form. (3)
 - (b) Explain the following parameters of an operational amplifier: (3)
 - (i) Input bias current
 - (ii) CMRR
 - (iii) Drift
 - (c) Calculate the output pulse width for the timer used as monostable multivibrator. Given, $R = 15K\Omega$ and $C = 0.22\mu F$. Find the value of C if pulse width changes to 20 ms. (3)
2. (A) Attempt **any two** of the following:
 - (a) Draw labelled diagram of Cathode Ray Tube (CRT) and explain each electrode in it. (3)
 - (b) Explain with the help of circuit diagram, working of Inductor input filter, when it is connected across the output terminals of a full-wave rectifier. Draw its output wave-form. (3)
 - (c) Draw block diagram IC 555. Explain function of each block. (3)
- (B) Attempt **any one** of the following:
 - (a) Draw a circuit diagram of an Inverting amplifier using Op-amplifier. Explain concept of virtual ground and hence derive the expression for its output voltage. (4)
 - (b) What is Amplitude Modulation? State the expression for modulated wave and draw the waveform of modulated wave. (4)
3. (A) Attempt **any two** of the following:
 - (a) With the help of Block diagram, explain the working of function Generator. (3)
 - (b) Draw the circuit diagram of a voltage regulator using Zener diode, explain its working. (3)
 - (c) In an Op-Amp Inverting adder, $V_1 = 0.2$ volt, $V_2 = 0.1$ volt, $V_3 = 0.4$ volt, $R_1 = 1K\Omega$, $R_2 = 2K\Omega$, $R_3 = 4K\Omega$. Find the output voltage if feed back resistance is $20K\Omega$. (3)



- (B) Attempt **any one** of the following:
- Explain the working of LVDT as a transducer. Draw neat diagram. State it's two applications. (4)
 - What do you mean by Network Topology? Explain Star, Ring and Bus Topology. (4)
4. (A) Attempt **any two** of the following:
- State any three front panel controls of CRO and give use of each control. (3)
 - Explain with diagram and wave form working of R-C filter for reducing ripple. (3)
 - Explain the working of differentiator circuit using operational amplifier. Derive expression for output voltage. (3)
- (B) Attempt **any one** of the following:
- Draw basic circuit for Schmitt trigger using Op-Amp. and explain the terms: (4)
 - UTP
 - LTP
 - Hysteresis
 - Draw a block-diagram showing basic elements of a Fiber Optical Communication System. Explain function of each block in brief. (4)
5. (A) Attempt **any two** of the following:
- Explain electro-static focussing system of a CRT (Cathodes Ray Tube). (3)
 - In Full Wave Rectifier, if primary of transformer is connected to 230V, 50 Hz and secondary voltage is 12-0-12V. (3)

Calculate:

 - Output DC voltage
 - PIV of the diode
 - Output ripple frequency
 - Give any three advantages of FM over AM. (3)

(Frequency Modulation and Amplitude Modulation)
- (B) Attempt **any one** of the following:
- State Active Transducers. Explain Optocoupler. (4)
 - How Op-amplifier can be used as a Subtractor? (4)
- OR**
5. (A) Attempt **any two** of the following:
- Explain the use of CRO for measurement of phase. (3)
 - Explain how Op-amplifier is used as a Buffer. Draw suitable circuit diagram. (3)
 - Explain how IC 555 can be used as a Pulse Position Modulator (PPM). (3)
- (B) Attempt **any one** of the following:
- Explain any four characteristics of a Power Supply. (4)
 - Draw general block-diagram of a pulsed radar and explain function of each block in brief. (4)